Accessing GPIO pins on Raspberry Pi

e-Yantra Team
Embedded Real-Time Systems Lab
Indian Institute of Technology-Bombay

IIT Bombay
July 4, 2016

What is GPIO?

What is GPIO?

1. Stands for General Purpose Input Output where external hardware can be connected

What is GPIO?

1. Stands for General Purpose Input Output where external hardware can be connected
2. The external hardware can be the input or output device

What is GPIO?

1. Stands for General Purpose Input Output where external hardware can be connected
2. The external hardware can be the input or output device
   - Input Device

     Example: Switch, Sensors, Keyboard etc...

What is GPIO?

1. Stands for General Purpose Input Output where external hardware can be connected
2. The external hardware can be the input or output device
   - Input Device

     Example: Switch, Sensors, Keyboard etc...
   - Output Device

     Example: Buzzer, LCD, Motors, LED etc...

Raspberry Pi Pinouts

Raspberry Pi Pinouts

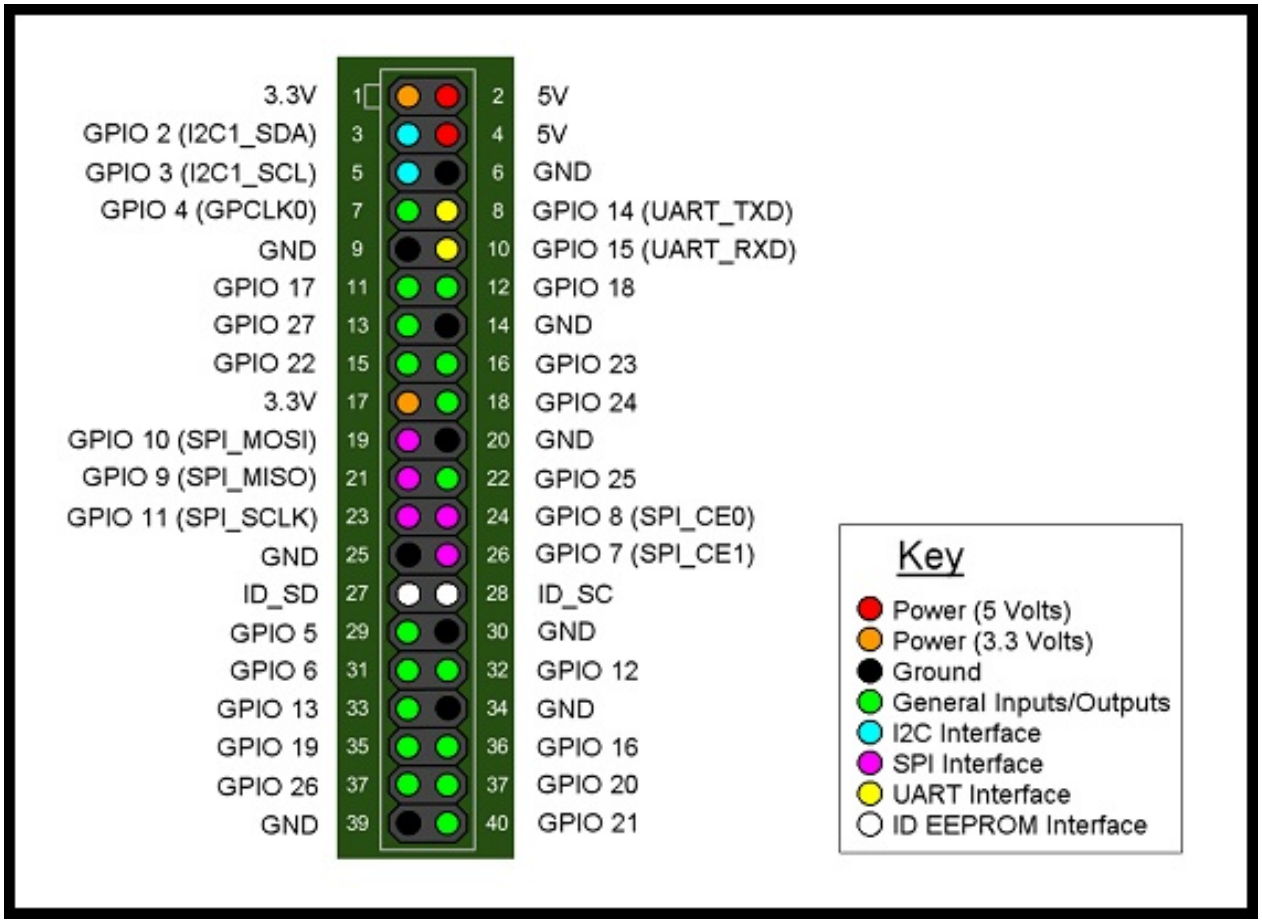

Experiment

Experiment

Interfacing an LED with the Raspberry Pi.

Hardware Required for the experiments:

Hardware Required for the experiments:

1. Breadboard

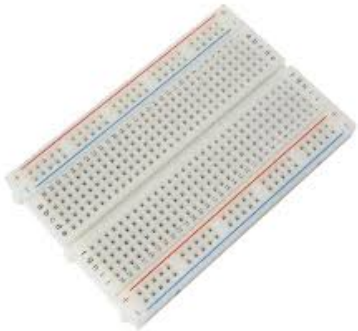

Hardware Required for the experiments:

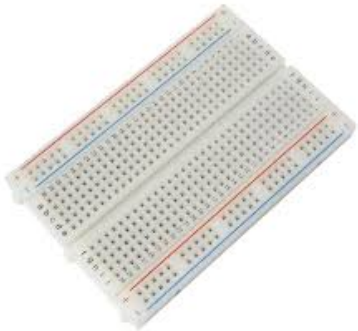

1. Breadboard

2. LED

Hardware Required for the experiments:

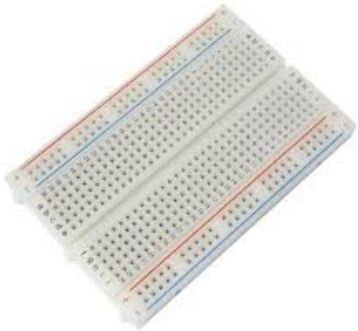

1. Breadboard

2. LED

3. 330 ohm resistor

Connections:

1. Anode of the LED is connected to pin no. 35 (i.e. GPIO 19 pin)

Connections:

1. Anode of the LED is connected to pin no. 35 (i.e. GPIO 19 pin)
2. Cathode of the LED is connected to a resistor(330 ohms) which is in turn connected to GND pin on R-Pi.

1. Figure shows the connections of LED and Raspberry Pi.

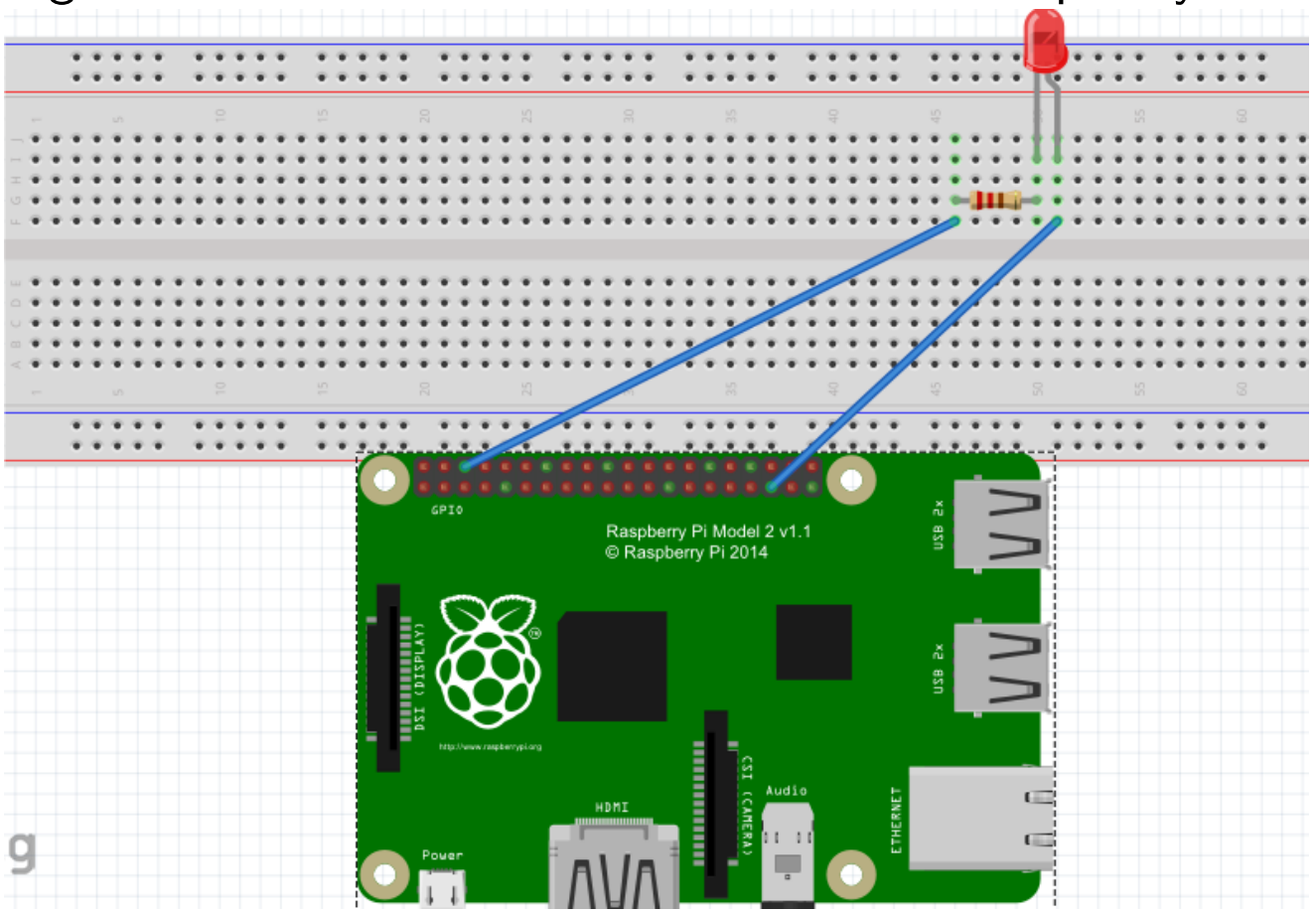

Problem Statement

Turn on the LED for 1 second and then turn it off for 1 second and repeat the process continuously.

Exercise

Exercise

Controlling a led using a push button

Thank You!

Post your queries on: http://qa.e-yantra.org/